

IV Semester B.Sc. Examination, May 2016  
(CBCS) (2015-16 and Onwards) (Fresh)  
ELECTRONICS – IV  
Digital Electronics and Verilog

Time : 3 Hours

Max. Marks : 70

**Instructions :** Answer all the questions from Part – A, any five questions from Part – B and any four questions from Part – C.

**Note :** It is required to answer all the questions of Part – A in any one page and to be answered only once. In this Part, answering the same question multiple times will not be considered for Evaluation.

## PART – A

Answer all the subdivisions :

(15×1=15)

1. i) The output of an OR gate is LOW
  - a) when all inputs are LOW
  - b) all the time
  - c) when all inputs are HIGH
  - d) when any input is LOW
- ii) A CMOS IC operating with a 3-volt supply will consume
  - a) more power than TTL
  - b) less power than TTL
  - c) same power as TTL
  - d) no power is consumed
- iii) The output pin numbers of the gates in IC 7400 are
  - a) 3, 6, 10 and 13
  - b) 3, 6, 11 and 8
  - c) 3, 5, 10 and 13
  - d) 3, 5, 11 and 8
- iv) If 1 and 1 are the inputs to Half adder circuit the result is
  - a) Sum-1 Carry-0
  - b) Sum-1 Carry-1
  - c) Sum-0 Carry-1
  - d) Sum-0 Carry-0
- v) Which one of the following can be used as parallel to serial convertor ?
  - a) Decoder
  - b) De multiplexer
  - c) Digital counter
  - d) Multiplexer

P.T.O.



vi) In a 4-variable K-map identify the 3 adjacent min. terms for the min. term X to form a quad.

- a)  $\overline{A}\overline{B}\overline{C}\overline{D}$ ,  $\overline{A}\overline{B}C\overline{D}$ ,  $A\overline{B}\overline{C}\overline{D}$       b)  $\overline{A}\overline{B}C\overline{D}$ ,  $ABC\overline{D}$ ,  $A\overline{B}C\overline{D}$   
 c)  $\overline{A}\overline{B}\overline{C}\overline{D}$ ,  $A\overline{B}\overline{C}\overline{D}$ ,  $ABC\overline{D}$       d)  $\overline{A}\overline{B}\overline{C}\overline{D}$ ,  $ABC\overline{D}$ ,  $A\overline{B}C\overline{D}$

	$\overline{C}\overline{D}$	$\overline{C}D$	$CD$	$C\overline{D}$
$\overline{A}\overline{B}$	X			
$\overline{A}B$				
$AB$				
$A\overline{B}$				

- vii) In a 4-bit binary weighted resistor type D/A converter least significant bit resistor is 200 K $\Omega$ . The resistor used for the most significant bit is  
 a) 100 K $\Omega$       b) 50 K $\Omega$   
 c) 12.5 K $\Omega$       d) 800 K $\Omega$
- viii) A J-K flip-flop with J = 0, K = 1 and a clock frequency of 10 KHz as input, then the Q output is  
 a) always at high state      b) always at low state  
 c) a 10 KHz square wave      d) a 5 KHz square wave
- ix) The content of a 4-bit register is 1101. The register is shifted 2 times to the right. The content of the register will be  
 a) 1011      b) 0011  
 c) 0010      d) 0111
- x) In order to build a mod-13 counter the minimum number of flip flops required are  
 a) 2      b) 4  
 c) 3      d) 5



- xi) Verilog HDL has the following basic values
- |                 |               |
|-----------------|---------------|
| a) 0, 0.5, 1, 5 | b) x, 2, 1, 0 |
| c) 0, 1, 0.5, z | d) 0, 1, z, x |
- xii) Which level of abstraction level is available in Verilog but not in VHDL ?
- |                     |                    |
|---------------------|--------------------|
| a) Behavioral level | b) Data flow level |
| c) Gate level       | d) Switch level    |
- xiii) In Verilog `h1AZ` is a
- |                              |                                     |
|------------------------------|-------------------------------------|
| a) 16 bit hexadecimal number | b) 32 bit hexadecimal number        |
| c) 4 bit hexadecimal number  | d) It is a sized hexadecimal number |
- xiv) If  $A = 4'b0011$  and  $B = 4'b'0100$ , then the result of  $A + B$  will be
- |         |         |
|---------|---------|
| a) 0110 | b) 0001 |
| c) 0111 | d) 1100 |
- xv) If time scale is defined as `timescale 10ns/1ns` and `#1.55 a = b`; then 'a' gets 'b' after
- |            |          |
|------------|----------|
| a) 10 ns   | b) 11 ns |
| c) 15.5 ns | d) 16 ns |

#### PART – B

Answer **any five** questions :

(5×7=35)

- a) State and prove DeMorgan's theorems with the help of truth tables.

b) Define the terms rise time, fall time and duty cycle with respect to a practical pulse. (4+3)
- a) What is Half subtractor ? Draw the circuit diagram using logic gates and write its truth table.

b) What is a demultiplexer ? Draw the logic diagram of 1 : 4 demultiplexer. (4+3)
- a) With a relevant circuit diagram, explain the working of 4-bit binary weighted D to A converter.

b) Differentiate between combinational and sequential logic circuits. (5+2)
5. Explain the working of clocked RS flip-flop with circuit diagram using only NAND gate. Draw the truth table and timing diagram. 7




6. a) Draw the logic diagram, truth table and timing diagram of asynchronous 3-bit up counter. (6+1)
- b) What is a Ring Counter ? 7
7. Define a module. Write a module for full adder circuit. 7
8. Explain logical and reduction operators in Verilog with examples. 7
9. Explain initial and always statements in behavioral modeling. 7

## PART – C

Answer **any four** questions : (4×5=20)

 10. Write the Boolean expression for the output Y in the given logic diagram by mentioning the output at the end of each gate and simplify it using Boolean laws. 5



11. Simplify the Boolean function  $f(A, B, C, D) = \sum m(1, 2, 5, 7, 9, 10, 15) + d(0, 3, 11, 12)$  using K-map and realize the simplified expression using basic gates. 5
12. A 4-bit Digital to Analog Converter has a step size of 0.75 V. Determine full scale output voltage and percentage of resolution. 5
13. Design a synchronous mod-3 counter using K-map technique. 5
14. Write a Verilog code for Binary to gray code and vice versa. 5
15. Write a Verilog code for 3 : 8 decoder. 5