



QP – 221

Third Semester B.Sc. Examination, April/May 2021

(F+R) (CBCS) (2017 – 18 and Onwards)

PHYSICS – III

Electricity and Magnetism

Time : 3 Hours

Max. Marks : 70

- Instructions :** i) Answer **any five** questions from **each Part**.  
ii) Non programmable scientific calculators are **allowed**.

PART – A

Answer **any five** questions. **Each** question carries **eight** marks. (5×8=40)

1. State and prove superposition theorem. (5×8=40)
2. a) Discuss the decay of charge in C-R circuit, hence define time constant. Represent the same graphically.  
b) Derive an expression for energy stored in an inductor. (5+3=8)
3. a) State and explain Biot-Savart's law.  
b) Derive an expression for torque on a current loop placed in a uniform magnetic field. (3+5=8)
4. a) Mention the conditions for moving coil galvanometer to be dead beat and ballistic.  
b) Explain how a BG can be used to determine high resistance by leakage. (2+6=8)
5. a) State and explain Stoke's theorem.  
b) Derive Maxwell's equation  $\nabla \times \vec{E} = -\frac{\partial \vec{B}}{\partial t}$  and discuss the physical significance. (2+6=8)
6. a) Define Poynting vector.  
b) Show that electromagnetic waves are transverse in nature. (2+6=8)
7. a) Mention the conditions under which AC bridges balanced.  
b) Derive an expression for self inductance of a coil using Maxwell's bridge. (3+5=8)
8. a) What is Thomson effect ? Distinguish between positive and negative effects.  
b) How do you calculate the value of Thomson coefficient from thermo-electric diagram ? (3+5=8)


P.T.O.



## PART – B

Solve **any five** problems. **Each** problem carries **four** marks.

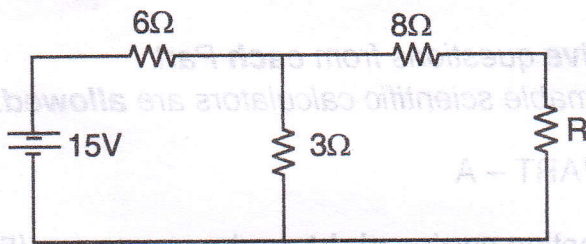9. Calculate the value of  $R$  for maximum power to transfer and the maximum power delivered to it.



10. A coil of self inductance  $10\text{ H}$  is in series with a resistance of  $100\ \Omega$ , connected to a  $100\text{ V}$  dc supply. Calculate the time constant and instantaneous current after time interval of  $0.1\text{ s}$ .
11. An electron after being accelerated through a p.d. of  $15\text{ kV}$ , enters a uniform magnetic field of  $0.04\text{ T}$ , perpendicular to its direction of motion. Calculate the radius of curvature of its trajectory [ $e = 1.6 \times 10^{-19}\text{ C}$ ,  $m = 9.1 \times 10^{-31}\text{ kg}$ ].
12. A long solenoid of length  $1\text{ m}$  and radius of cross section  $1.5\text{ cm}$  has five layers of windings  $850$  turns each. If the solenoid carries current of  $6\text{ A}$ , calculate the value of magnetic field and magnetic flux through cross section at its centre.
13. Find the divergence of  $\vec{A}$  at a point  $(1, -1, 1)$  where  $\vec{A} = x^2z\hat{i} - 2y^3z^2\hat{j} + xy^2z\hat{k}$ .
14. If the electric field between a parallel plate air capacitor of area  $1.5\text{ m}^2$  changes at the rate of  $10^6\text{ Vm}^{-1}\text{ s}^{-1}$ , calculate the displacement current.
15. A capacitor  $2\ \mu\text{F}$  and a resistor are connected to  $240\text{ V}$ ,  $50\text{ Hz}$  ac in series. If the p.d. across resistor is equal to p.d. across capacitor. Calculate the resistance of the coil.
16. The thermo emf of a thermocouple in microvolts is given by the equation  $e = 16.34\theta - 0.021\theta^2$  when the junctions are at  $0^\circ\text{C}$  and  $\theta^\circ\text{C}$ . Calculate  
 i) thermo electric power at  $100^\circ\text{C}$ .  
 ii) the peltier emf at  $100^\circ\text{C}$ .



PART - C

17. Answer **any five** questions. **Each** question carries **two** marks. (5×2=10)

- a) Is it possible to construct ideal voltage source ? Explain.
- b) Is the law of conservation of energy violated due to production of back emf in L-R circuit ? Explain.
- c) Does an electric charge kept near a strong magnet experience force ? Explain.
- d) What is the advantage of having two coils in Helmholtz tangent galvanometer ?
- e) When is the given vector function irrotational ? Explain.
- f) How does the displacement current changes, when the applied frequency is changed in a capacitor ?
- g) Does resonant frequency of series LCR circuit depends upon resistance ? Explain.
- h) Does thermo-electric effect obey the law of conservation of energy ?