



## III Semester B.Sc. Examination, April/May 2021

(CBCS) (F+R) (2015 – 16 and Onwards)

## ELECTRONICS – III

## Linear ICs and C Programming

Time : 3 Hours

Max. Marks : 70

- Instructions :**
- Answer **all** the questions from Part – A, **any five** questions from Part – B, **any four** questions from Part – C.
  - Answer **all** questions of Part – A in **any one** page, **same** questions answered multiple times will **not** be considered for evaluation.

## PART – A

1. Answer **all** the sub-divisions.

(15×1=15)

- \_\_\_\_\_ is used as dielectric for capacitor in IC fabrication.
  - Hydrochloric acid
  - Formaldehyde
  - Carbon dioxide
  - Silicon dioxide
- The differential gain of an Op-Amp is
  - very high
  - very low
  - dependent on input voltage .
  - about 100
- The ideal Op-Amp has the following characteristics
  - $R_i = \infty, A = \infty, R_o = 0$
  - $R_i = 0, A = \infty, R_o = 0$
  - $R_i = \infty, A = \infty, R_o = \infty$
  - $R_i = 0, A = \infty, R_o = \infty$
- \_\_\_\_\_ type of amplifier has output voltage equal to the negative average of all input voltages.
  - Non-inverting averaging amplifier
  - Inverting averaging amplifier
  - Non-inverting summing amplifier
  - None of these
- An oscillator circuit converts
  - a.c. power into d.c. power
  - d.c. power into a.c. power
  - mechanical power into a.c. power
  - none of these

P.T.O.





- vi) In phase shift oscillator, the total phase shift produced by three RC networks is
- a)  $90^\circ$
  - b)  $360^\circ$
  - c)  $180^\circ$
  - d)  $270^\circ$
- vii) A multivibrator is an electronic circuit used to implement
- a) Oscillator
  - b) Timer
  - c) Flip-flop
  - d) All of these
- viii) A structure contains
- a) Arrays of individual members
  - b) Individual structures as its elements
  - c) Structure variables
  - d) Structure members
- ix) All keywords in C are in
- a) Lower case letters
  - b) Upper case letters
  - c) Camel case letters
  - d) None of the mentioned
- x) \_\_\_\_\_ is correct with respect to the size of the data types.
- a)  $\text{char} > \text{int} > \text{float}$
  - b)  $\text{int} > \text{char} > \text{float}$
  - c)  $\text{double} > \text{char} > \text{int}$
  - d)  $\text{char} < \text{int} < \text{double}$
- xi) The C code 'for (;)' represents an infinite loop. It can be terminated by
- a) break
  - b) exit(0)
  - c) abort()
  - d) terminate
- xii) \_\_\_\_\_ is an example of iteration in C.
- a) for
  - b) while
  - c) do-while
  - d) all of the mentioned
- xiii) \_\_\_\_\_ is a correct format for declaration of function.
- a) return-type function-name (argument type);
  - b) argument-type function-name (return type) {}
  - c) return-type (argument type) function-name;
  - d) all of the mentioned





- xiv) \_\_\_\_\_ operation is illegal in structures.
  - a) Typecasting of structure
  - b) Pointer to a variable of the same structure
  - c) Dynamic allocation of memory for structure
  - d) All of the mentioned
  
- xv) The size of a union is determined by the size of the
  - a) First member in the union
  - b) Last member in the union
  - c) Biggest member in the union
  - d) Sum of the sizes of all members

PART - B

Answer **any five** questions. (5×7=35)

- 2. a) Give the classification of ICs.
- b) Explain the fabrication process of a transistor with relevant diagrams. (2+5)
  
- 3. a) Draw the block diagram of the Op-Amp and explain the function of each block.
- b) Define CMRR and slew rate with respect to Op-Amp. (5+2)
  
- 4. a) Obtain the expression for the voltage gain of an Op-Amp inverting amplifier.
- b) Draw the circuit diagram of Op-Amp comparator. (5+2)
  
- 5. a) Explain the operation of high pass filter using Op-Amp with relevant circuit diagram.
- b) Mention any two fixed IC regulators. (5+2)
  
- 6. a) Draw the circuit diagram of phase shift oscillator and explain its working.
- b) Draw the functional block diagram of IC-555 timer. (4+3)
  
- 7. a) Explain any two data types in C.
- b) Mention the arithmetic operators in C programming. (4+3)
  
- 8. What is an array ? Write a program to read and print a two dimensional array. 7
  
- 9. Explain the *while* and *for* looping techniques in C with examples. 7





PART - C


Answer any four questions.

(4x5=20)

10. Calculate the output voltage in the circuit given below.

5

$V_{CC} = 15V, V_{EE} = -15V$

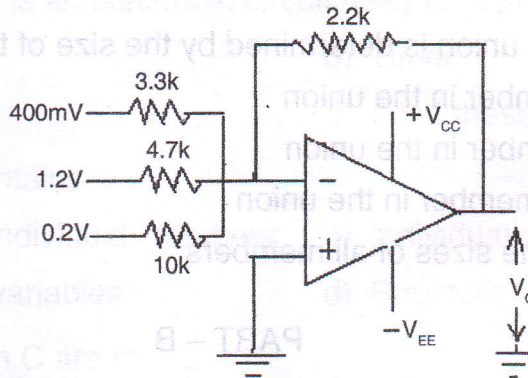

11. In a Wein bridge oscillator,  $R = 2\text{ K}\Omega$ ,  $C = 0.1\ \mu\text{F}$ , calculate the frequency of the output waveform. Draw the relevant circuit diagram.

5

12. Design a low pass filter at a cut off frequency of 4 KHz with pass band gain of 2. Choose  $C = 0.01\ \mu\text{F}$  and  $R_F = 100\text{ K}\Omega$ .

5

13. Write a C program to generate prime numbers up to an integer N.

5

14. Write a C program to find minimum and maximum of N numbers.

5

15. Write a C program to find the sum of two matrices of order  $M \times N$ .

5