



QP – 255

I Semester B.Sc. Examination, April/May 2021  
(CBCS – F + R – 2014-15 and Onwards)  
**ELECTRONICS – I**  
**Basic Electronics**

Time : 3 Hours

Max. Marks : 70

- Instructions :**
- Answer **all** questions from Part – A, **any five** questions from Part – B and **any four** questions from Part – C.
  - Answer **all** questions of Part – A in **any one** page, the **same** questions answered multiple times will **not** be considered for evaluation.

PART – A

1. Answer **all** the sub-divisions :

(1×15=15)

- A resistor has colour code bands as Brown, Black, Orange and Gold. Its value is
  - $1\text{ K}\Omega \pm 10\%$
  - $10\text{ K}\Omega \pm 5\%$
  - $100\text{ K}\Omega \pm 10\%$
  - $1\text{ M}\Omega \pm 10\%$
- Internal resistance of an ideal current source is
  - Zero
  - Infinity
  - $0.5\text{ M}\Omega$
  - High
- In a pure inductive circuit
  - The current is in phase with the voltage
  - The current lags behind the voltage by  $90^\circ$
  - The current leads the voltage by  $90^\circ$
  - The current can lead or lag by  $90^\circ$
- In a step down transformer, the number of turns in the secondary coil is
  - Less than primary coil turns
  - More than primary coil turns
  - Equal to primary coil turns
  - None of these
- According to Kirchhoffs Current Law, the algebraic sum of the currents meeting at a point is always
  - Zero
  - Positive
  - Negative
  - Equal to unity

P.T.O.





PART - B

Answer **any five** questions :

(5×7=35)

- 2. a) With a neat circuit diagram, explain the growth of charge in a series RC circuit excited by a DC source. Define 'Time constant' of this circuit.  
b) What are active and passive components ? Give examples. (5+2)
- 3. a) When does a practical voltage source behave like a good voltage source ?  
b) State Thevenin's Theorem. With suitable circuit diagrams, explain the steps to Thevenise a resistive network. (2+5)
- 4. a) Write the three approximations of a diode.  
b) Draw the V-I characteristics of a diode. Define : Knee voltage. (3+4)
- 5. a) With the help of circuit diagram and waveforms, explain half wave rectifier in detail.  
b) Draw the circuit diagram of transistor voltage regulator. (5+2)
- 6. a) Draw the output characteristics of a transistor in CE configuration and explain its different regions.  
b) Define the terms ' $\alpha$ ' and ' $\beta$ ' for a transistor. (5+2)
- 7. a) Draw the circuit diagram of voltage divider biasing circuit.  
b) With necessary diagram, explain the working of JFET. (2+5)
- 8. a) With an example, explain how a decimal number is converted to its equivalent binary code. Consider the integer and fractional parts of decimal number.  
b) Write the BCD code for all decimal digits. (4+3)
- 9. With an example, explain binary subtraction using 2's complement method. 7

PART - C

Answer **any four** questions :


(4×5=20)

- 10. A-series resonance circuit has a resistor of 50  $\Omega$ , inductor of 50 mH and capacitor of 2nF. Calculate :
  - i) Resonant frequency
  - ii) Bandwidth when Q factor is 100.




11. Draw the Thevenin's equivalent circuit for the circuit given below. Find the current through and voltage across  $R_L = 5\Omega$ .

5

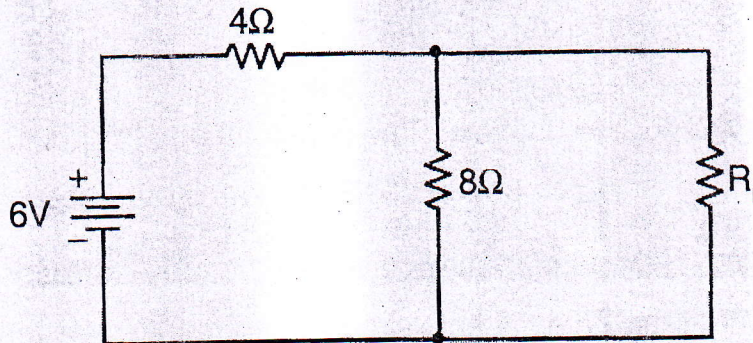

12. Determine the value of  $R_L$  for maximum power transfer in the given circuit. Also calculate the maximum power delivered to the load.

5

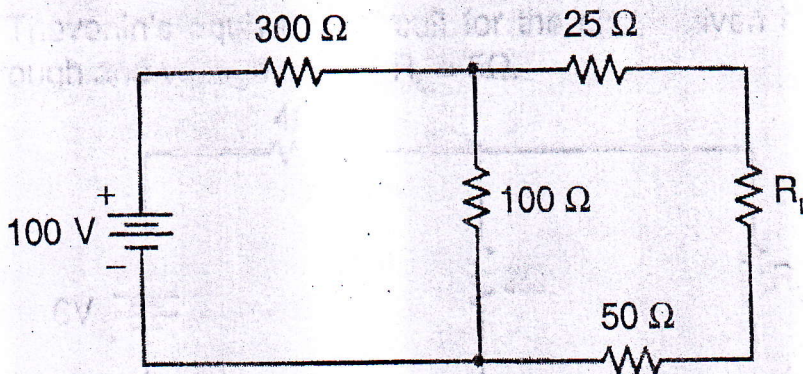

13. A transformer used in a half wave rectifier has a turn's ratio of 8 : 1. The primary is connected to 220 V, 50 Hz. Assuming the diode to be ideal, Calculate:

- i) The DC output voltage of the rectifier
- ii) Average current
- iii) PIV of the rectifier diode.

5

14. The following values are recorded to plot an NPN transistor characteristics in CE mode. Determine  $r_i$ ,  $r_o$  and  $\beta_{ac}$  from those values.

5

| $V_{BE}$ (volt) | $I_B$ ( $\mu$ A) | $V_{CE}$ (volt) | $I_C$ (mA) |
|-----------------|------------------|-----------------|------------|
| 0.625           | 25               | 5               | 2.5        |
| 0.675           | 125              | 5               | 12.5       |
| 0.675           | 125              | 10              | 13         |

15. Convert the following numbers accordingly.

(3+2)

a)  $42_{(10)} = \underline{\hspace{2cm}}_{(2)} = \underline{\hspace{2cm}}_{(16)}$

b)  $7E_{(16)} = \underline{\hspace{2cm}}_{(10)} = \underline{\hspace{2cm}}_{(2)}$